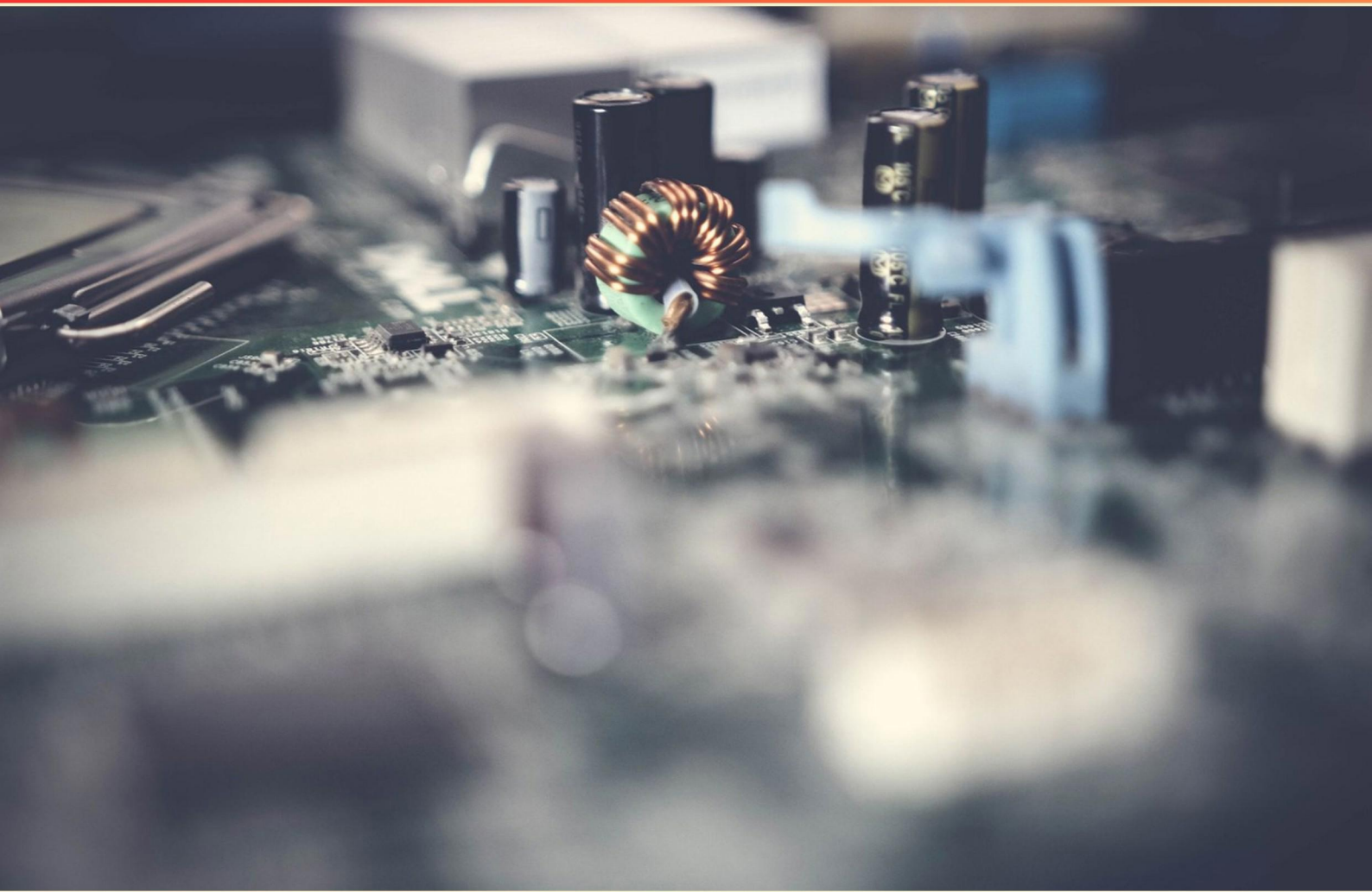


ELECTRICAL COMPREHENSION DAA PRACTICE TEST (SAMPLE)

STUDY GUIDE



**SAMPLE STUDY GUIDE
WITH LIMITED QUESTIONS**

**VISIT US ONLINE FOR
THE FULL VERSION STUDY GUIDE**

<https://electricalcompdaa.examzify.com>



Copyright © 2026 by Examzify - A Kaluba Technologies Inc. product.

ALL RIGHTS RESERVED.

No part of this book may be reproduced or transferred in any form or by any means, graphic, electronic, or mechanical, including photocopying, recording, web distribution, taping, or by any information storage retrieval system, without the written permission of the author.

Notice: Examzify makes every reasonable effort to obtain accurate, complete, and timely information about this product from reliable sources.

SAMPLE

Table of Contents

Copyright	1
Table of Contents	2
Introduction	3
How to Use This Guide	4
Questions	5
Answers	8
Explanations	10
Next Steps	15

SAMPLE

Introduction

Preparing for a certification exam can feel overwhelming, but with the right tools, it becomes an opportunity to build confidence, sharpen your skills, and move one step closer to your goals. At Examzify, we believe that effective exam preparation isn't just about memorization, it's about understanding the material, identifying knowledge gaps, and building the test-taking strategies that lead to success.

This guide was designed to help you do exactly that.

Whether you're preparing for a licensing exam, professional certification, or entry-level qualification, this book offers structured practice to reinforce key concepts. You'll find a wide range of multiple-choice questions, each followed by clear explanations to help you understand not just the right answer, but why it's correct.

The content in this guide is based on real-world exam objectives and aligned with the types of questions and topics commonly found on official tests. It's ideal for learners who want to:

- Practice answering questions under realistic conditions,
- Improve accuracy and speed,
- Review explanations to strengthen weak areas, and
- Approach the exam with greater confidence.

We recommend using this book not as a stand-alone study tool, but alongside other resources like flashcards, textbooks, or hands-on training. For best results, we recommend working through each question, reflecting on the explanation provided, and revisiting the topics that challenge you most.

Remember: successful test preparation isn't about getting every question right the first time, it's about learning from your mistakes and improving over time. Stay focused, trust the process, and know that every page you turn brings you closer to success.

Let's begin.

How to Use This Guide

This guide is designed to help you study more effectively and approach your exam with confidence. Whether you're reviewing for the first time or doing a final refresh, here's how to get the most out of your Examzify study guide:

1. Start with a Diagnostic Review

Skim through the questions to get a sense of what you know and what you need to focus on. Your goal is to identify knowledge gaps early.

2. Study in Short, Focused Sessions

Break your study time into manageable blocks (e.g. 30 – 45 minutes). Review a handful of questions, reflect on the explanations.

3. Learn from the Explanations

After answering a question, always read the explanation, even if you got it right. It reinforces key points, corrects misunderstandings, and teaches subtle distinctions between similar answers.

4. Track Your Progress

Use bookmarks or notes (if reading digitally) to mark difficult questions. Revisit these regularly and track improvements over time.

5. Simulate the Real Exam

Once you're comfortable, try taking a full set of questions without pausing. Set a timer and simulate test-day conditions to build confidence and time management skills.

6. Repeat and Review

Don't just study once, repetition builds retention. Re-attempt questions after a few days and revisit explanations to reinforce learning. Pair this guide with other Examzify tools like flashcards, and digital practice tests to strengthen your preparation across formats.

There's no single right way to study, but consistent, thoughtful effort always wins. Use this guide flexibly, adapt the tips above to fit your pace and learning style. You've got this!

Questions

SAMPLE

- 1. What term describes a basic schematic showing how components are connected?**
 - A. Battery
 - B. Circuit symbol for battery
 - C. Ammeter
 - D. Simple circuit diagram
- 2. If you double the resistance of one branch in parallel, what happens to that branch's current?**
 - A. It doubles
 - B. It halves
 - C. It remains the same
 - D. It goes to zero
- 3. Which statement correctly explains why longer wires have higher resistance?**
 - A. The longer path increases collisions
 - B. The material changes along the length
 - C. The longer wire is heavier
 - D. Electrons collide with more ions over the longer path
- 4. In a series circuit, the sum of the potential differences across all components equals the battery's total potential difference?**
 - A. The current
 - B. The cell's total potential difference
 - C. The resistance
 - D. The sum of the potential differences across all components
- 5. In bright light, what happens to the resistance of an LDR?**
 - A. High
 - B. Zero
 - C. Infinite
 - D. Low

- 6. Which term describes a material that can carry an electric current and may also conduct heat?**
- A. Insulator
 - B. Conductor
 - C. Semiconductor
 - D. Dielectric
- 7. As more components are added in series, what happens to total resistance?**
- A. Oscillates
 - B. Decreases
 - C. Stays the same
 - D. Increases
- 8. In a series circuit, if you add more resistors, the current decreases?**
- A. Current increases
 - B. Current decreases
 - C. Current stays the same
 - D. Current becomes negative
- 9. Which statement best describes conductors and insulators?**
- A. Metals are insulators; rubber and plastics are conductors
 - B. Water is always an insulator
 - C. Metals are conductors; rubber and plastics are insulators
 - D. Wood is a conductor; glass is an insulator
- 10. If one component in parallel circuit breaks, others still work?**
- A. They stop
 - B. The circuit opens
 - C. Other components work
 - D. They burn out

Answers

SAMPLE

1. D
2. B
3. D
4. D
5. D
6. B
7. D
8. B
9. C
10. C

SAMPLE

Explanations

SAMPLE

1. What term describes a basic schematic showing how components are connected?

- A. Battery
- B. Circuit symbol for battery
- C. Ammeter

D. Simple circuit diagram

A simple circuit diagram describes a basic schematic showing how components are connected. It uses standard symbols for each component and lines to show the electrical connections, focusing on the wiring path rather than physical layout. A battery is a power source, and its circuit symbol is the graphical representation used inside diagrams. An ammeter is a device to measure current. Those are parts or symbols used within diagrams, but they don't define the type of diagram itself. So the term that best fits a basic schematic showing how components are connected is a simple circuit diagram.

2. If you double the resistance of one branch in parallel, what happens to that branch's current?

- A. It doubles
- B. It halves**
- C. It remains the same
- D. It goes to zero

In a parallel circuit, the voltage across each branch is the same, and the branch current follows $I = V/R$. If you double the resistance of one branch while the supply voltage stays fixed, that branch's current becomes $I' = V/(2R) = (1/2)(V/R)$. So the current in that branch is halved. The other branches see the same voltage and are unaffected by this change in the first branch, though the total current drawn from the source would decrease accordingly.

3. Which statement correctly explains why longer wires have higher resistance?

- A. The longer path increases collisions
- B. The material changes along the length
- C. The longer wire is heavier

D. Electrons collide with more ions over the longer path

Resistance in a metal comes from electrons colliding with the lattice ions and losing energy as heat. In a longer wire, electrons must travel a greater distance, so they encounter more ions along the way. Each collision transfers some electric energy to the lattice, so the total energy lost per unit charge increases with length. That's why resistance grows with length (and, for a given material, is proportional to L and inversely proportional to cross-sectional area, $R = \rho L/A$). The idea that the longer path means more collisions with ions is the precise reason the resistance is higher. The other ideas—changes in material along the length or the wire simply being heavier—don't explain the electrical resistance in the same direct way.

4. In a series circuit, the sum of the potential differences across all components equals the battery's total potential difference?

- A. The current
- B. The cell's total potential difference
- C. The resistance

D. The sum of the potential differences across all components

In a single-loop series circuit, Kirchhoff's voltage law applies: the sum of all voltage drops around the loop must equal the supply voltage. The battery provides a fixed total potential difference, and as the same current flows through every component, the voltage across each component adds up to that same total. In other words, the sum of the potential differences across all components equals the battery's total potential difference. The current and the resistance explain how that voltage is distributed ($V = IR$ tells you how much drop each component gets for the given current), but the fundamental idea here is that voltages around the loop add up to the source voltage.

5. In bright light, what happens to the resistance of an LDR?

- A. High
- B. Zero
- C. Infinite

D. Low

Light affects how well the material conducts electricity. An LDR is a semiconductor whose conductivity rises when illuminated. When bright light shines on it, photons generate more free charge carriers (electrons and holes), so the material conducts better. For a given applied voltage, more current flows, which means the resistance drops. It isn't literally zero or infinite in normal conditions, but it becomes much lower than in darkness. That's why the correct choice is that the resistance is low in bright light.

6. Which term describes a material that can carry an electric current and may also conduct heat?

- A. Insulator
- B. Conductor**
- C. Semiconductor
- D. Dielectric

Materials that can carry an electric current are called conductors. In metals, electrons are loosely bound and move freely, which allows electric current to flow easily. Those same free-moving electrons also transfer energy efficiently, so conductors are typically good at conducting heat as well. An insulator or dielectric resists electric current, so they don't fit the description. A semiconductor can conduct under certain conditions (like with doping or temperature changes), but not as readily as a true conductor. So the best fit for a material that can carry current and may also conduct heat is conductor.

7. As more components are added in series, what happens to total resistance?

- A. Oscillates
- B. Decreases
- C. Stays the same

D. Increases

When components are in series, their resistances simply add up. The total resistance is the sum of each component's resistance: $R_{\text{total}} = R_1 + R_2 + R_3 + \dots$. Adding another component with its own resistance increases that sum, so the overall resistance grows. This aligns with Ohm's law (for a fixed voltage, $I = V / R_{\text{total}}$): higher R_{total} means less current, which matches the intuitive idea that more obstacles to current flow raise the total resistance. If the added component happened to have zero resistance, the total would stay the same, but with real components that have positive resistance, the total increases.

8. In a series circuit, if you add more resistors, the current decreases?

- A. Current increases
- B. Current decreases**
- C. Current stays the same
- D. Current becomes negative

In a series circuit, the total resistance increases when you add more resistors, because the resistances add up. With a fixed supply voltage, current is $I = V / R_{\text{total}}$, so as R_{total} goes up, the current goes down. The same current flows through all elements in a series circuit, but its magnitude is reduced as you add resistance. It won't become negative or stay the same just from adding resistors. So the current decreases.

9. Which statement best describes conductors and insulators?

- A. Metals are insulators; rubber and plastics are conductors
- B. Water is always an insulator
- C. Metals are conductors; rubber and plastics are insulators**
- D. Wood is a conductor; glass is an insulator

Materials differ in how easily charges can move through them. Metals have many free electrons that drift readily when an electric field is applied, so they conduct electricity well. Rubber and plastics, on the other hand, hold their electrons tightly and have high resistance, making them insulators that resist current. Water's conductivity isn't fixed: it depends on dissolved ions, so pure water is a poor conductor while common tap water can conduct due to impurities. Wood and glass are also insulators. So the statement that metals are conductors and rubber and plastics are insulators matches the typical behavior of these materials.

10. If one component in parallel circuit breaks, others still work?

- A. They stop
- B. The circuit opens
- C. Other components work**
- D. They burn out

In a parallel circuit, each component has its own path across the same two nodes, so current can flow through the other branches even if one path breaks. If one component fails or its branch opens, that branch simply stops drawing current, but the remaining branches still have the full source voltage across them and continue to operate. That's why other components keep working when one branch breaks. This contrasts with a series arrangement, where a break stops the entire circuit.

SAMPLE

Next Steps

Congratulations on reaching the final section of this guide. You've taken a meaningful step toward passing your certification exam and advancing your career.

As you continue preparing, remember that consistent practice, review, and self-reflection are key to success. Make time to revisit difficult topics, simulate exam conditions, and track your progress along the way.

If you need help, have suggestions, or want to share feedback, we'd love to hear from you. Reach out to our team at hello@examzify.com.

Or visit your dedicated course page for more study tools and resources:

<https://electricalcompdaa.examzify.com>

We wish you the very best on your exam journey. You've got this!

SAMPLE