

# Independent Electrical Contractors (IEC) Year 2

## Part 3 Practice Test

### (Sample)

#### Study Guide



**Everything you need from our exam experts!**

**This is a sample study guide. To access the full version with hundreds of questions,**

**Copyright © 2026 by Examzify - A Kaluba Technologies Inc. product.**

**ALL RIGHTS RESERVED.**

**No part of this book may be reproduced or transferred in any form or by any means, graphic, electronic, or mechanical, including photocopying, recording, web distribution, taping, or by any information storage retrieval system, without the written permission of the author.**

**Notice: Examzify makes every reasonable effort to obtain from reliable sources accurate, complete, and timely information about this product.**

**SAMPLE**

# Table of Contents

<b>Copyright</b> .....	<b>1</b>
<b>Table of Contents</b> .....	<b>2</b>
<b>Introduction</b> .....	<b>3</b>
<b>How to Use This Guide</b> .....	<b>4</b>
<b>Questions</b> .....	<b>6</b>
<b>Answers</b> .....	<b>9</b>
<b>Explanations</b> .....	<b>11</b>
<b>Next Steps</b> .....	<b>17</b>

SAMPLE

# Introduction

Preparing for a certification exam can feel overwhelming, but with the right tools, it becomes an opportunity to build confidence, sharpen your skills, and move one step closer to your goals. At Examzify, we believe that effective exam preparation isn't just about memorization, it's about understanding the material, identifying knowledge gaps, and building the test-taking strategies that lead to success.

This guide was designed to help you do exactly that.

Whether you're preparing for a licensing exam, professional certification, or entry-level qualification, this book offers structured practice to reinforce key concepts. You'll find a wide range of multiple-choice questions, each followed by clear explanations to help you understand not just the right answer, but why it's correct.

The content in this guide is based on real-world exam objectives and aligned with the types of questions and topics commonly found on official tests. It's ideal for learners who want to:

- Practice answering questions under realistic conditions,
- Improve accuracy and speed,
- Review explanations to strengthen weak areas, and
- Approach the exam with greater confidence.

We recommend using this book not as a stand-alone study tool, but alongside other resources like flashcards, textbooks, or hands-on training. For best results, we recommend working through each question, reflecting on the explanation provided, and revisiting the topics that challenge you most.

Remember: successful test preparation isn't about getting every question right the first time, it's about learning from your mistakes and improving over time. Stay focused, trust the process, and know that every page you turn brings you closer to success.

Let's begin.

# How to Use This Guide

**This guide is designed to help you study more effectively and approach your exam with confidence. Whether you're reviewing for the first time or doing a final refresh, here's how to get the most out of your Examzify study guide:**

## 1. Start with a Diagnostic Review

**Skim through the questions to get a sense of what you know and what you need to focus on. Don't worry about getting everything right, your goal is to identify knowledge gaps early.**

## 2. Study in Short, Focused Sessions

**Break your study time into manageable blocks (e.g. 30 - 45 minutes). Review a handful of questions, reflect on the explanations, and take breaks to retain information better.**

## 3. Learn from the Explanations

**After answering a question, always read the explanation, even if you got it right. It reinforces key points, corrects misunderstandings, and teaches subtle distinctions between similar answers.**

## 4. Track Your Progress

**Use bookmarks or notes (if reading digitally) to mark difficult questions. Revisit these regularly and track improvements over time.**

## 5. Simulate the Real Exam

**Once you're comfortable, try taking a full set of questions without pausing. Set a timer and simulate test-day conditions to build confidence and time management skills.**

## 6. Repeat and Review

**Don't just study once, repetition builds retention. Re-attempt questions after a few days and revisit explanations to reinforce learning.**

## 7. Use Other Tools

**Pair this guide with other Examzify tools like flashcards, and digital practice tests to strengthen your preparation across formats.**

**There's no single right way to study, but consistent, thoughtful effort always wins. Use this guide flexibly — adapt the tips above to fit your pace and learning style. You've got this!**

**SAMPLE**

## **Questions**

SAMPLE

- 1. When using a transformer, what is transferred from the primary to the secondary?**
  - A. Voltage**
  - B. Current**
  - C. Power**
  - D. Resistance**
- 2. Inductors in parallel add like resistors in \_\_\_\_.**
  - A. series**
  - B. parallel**
  - C. combination**
  - D. discrete**
- 3. What is an example of unsafe conditions on a construction site?**
  - A. Worn-out tools**
  - B. Properly trained workers**
  - C. Effective safety measures**
  - D. Working in a well-lit environment**
- 4. To power 120-volt loads only, how should the two secondary windings be connected?**
  - A. Series**
  - B. Parallel**
  - C. Direct**
  - D. Single**
- 5. What unit is apparent power measured in?**
  - A. Watts**
  - B. Volt-amps**
  - C. Kilowatts**
  - D. Ohms**

**6. In a large service installation, what type of transformers are contained within CT cans?**

- A. Factor transformers**
- B. Voltage transformers**
- C. Current transformers**
- D. Phase transformers**

**7. The peak-to-peak value of a sine wave is how many times the maximum positive peak value?**

- A. Once**
- B. Twice**
- C. Three times**
- D. Four times**

**8. What is the maximum phase angle between current and voltage in purely inductive or purely capacitive circuits?**

- A.  $45^\circ$**
- B.  $60^\circ$**
- C.  $90^\circ$**
- D.  $120^\circ$**

**9. Smaller transformers, typically 50 KVA and smaller, operating at or below 600 volts, are normally wound for what type of polarity?**

- A. Additive polarity**
- B. Subtractive polarity**
- C. Neutral polarity**
- D. Variable polarity**

**10. In a 60 Hz circuit with a 1.3 mH inductor, what is the inductive reactance in ohms after conversion?**

- A. 0.49**
- B. 0.25**
- C. 1.02**
- D. 3.14**

## **Answers**

SAMPLE

1. C
2. B
3. A
4. B
5. B
6. C
7. B
8. C
9. A
10. A

SAMPLE

## **Explanations**

SAMPLE

**1. When using a transformer, what is transferred from the primary to the secondary?**

- A. Voltage**
- B. Current**
- C. Power**
- D. Resistance**

In a transformer, the key principle is that it transfers power from the primary winding to the secondary winding through electromagnetic induction. This transfer occurs while maintaining the relationship of voltage and current based on the turns ratio of the transformer. When voltage is increased in the primary winding, the current decreases in the secondary, and vice versa, ensuring that the total power remains constant (neglecting losses). This means that while individual voltages and currents change based on the turns ratio, the overall power being transferred—calculated as the product of voltage and current—remains consistent across the transformer's primary and secondary windings. Resistance is not transferred, as it is a characteristic of the materials used in the windings rather than a parameter that changes hands during operation. Therefore, understanding that the fundamental function of a transformer is to transfer power helps clarify the operation and design of electrical systems where transformers are employed.

**2. Inductors in parallel add like resistors in \_\_\_\_.**

- A. series**
- B. parallel**
- C. combination**
- D. discrete**

When inductors are connected in parallel, their total inductance can be calculated in a manner similar to how resistances in parallel are combined. The formula for calculating the total inductance of inductors in parallel is given by:  $1 / L_{\text{total}} = 1 / L_1 + 1 / L_2 + 1 / L_3 + \dots + 1 / L_n$  This relationship mirrors the formula used for determining the total resistance in parallel circuits, which is:  $1 / R_{\text{total}} = 1 / R_1 + 1 / R_2 + 1 / R_3 + \dots + 1 / R_n$  Both inductors and resistors in parallel must be treated with this reciprocal relationship, resulting in a total that is less than the smallest individual value among them. This is why inductors in parallel add like resistors in parallel, reflecting a fundamental principle of circuit theory that applies across different types of components. Understanding this concept is crucial for electrical design and troubleshooting, as it allows for a clear and accurate assessment of circuit behavior.

### 3. What is an example of unsafe conditions on a construction site?

- A. Worn-out tools**
- B. Properly trained workers**
- C. Effective safety measures**
- D. Working in a well-lit environment**

Worn-out tools represent an unsafe condition on a construction site because they can increase the risk of accidents and injuries. Tools that are damaged or no longer functioning correctly may fail during use, potentially leading to severe injuries for workers. For example, a worn-out saw could bind or break, causing it to kick back unexpectedly, endangering the user and those nearby. In contrast, the other options describe conditions that contribute to safety. Properly trained workers are crucial for ensuring that safety protocols are followed and that all individuals on site know how to operate tools and handle hazardous materials safely. Effective safety measures, such as personal protective equipment (PPE) and safety training, are designed to minimize risks and protect workers. Similarly, working in a well-lit environment enhances visibility, making it easier to see potential hazards and operate equipment safely. Therefore, worn-out tools stand out as a clear example of unsafe conditions that could lead to accidents on a construction site.

### 4. To power 120-volt loads only, how should the two secondary windings be connected?

- A. Series**
- B. Parallel**
- C. Direct**
- D. Single**

For powering 120-volt loads, connecting the two secondary windings in parallel is the appropriate choice. When windings are connected in parallel, they match the voltage rating while allowing for increased current capacity. Each winding provides the same voltage, which maintains the 120 volts needed for the loads. In a parallel connection, if one winding is loaded, the other can assist in sharing the load, ensuring that the overall output remains stable at 120 volts. This configuration is particularly beneficial for maintaining proper voltage levels while powering multiple loads or when dealing with varying load conditions. Other connection types, such as series connections, would result in an increased voltage (in this case, 240 volts if both windings are 120 volts each), which is not suitable for 120-volt applications. The terms "direct" and "single" do not specifically indicate a valid electrical connection configuration relevant to this scenario. Therefore, parallel is the most effective and safe method for connecting the windings to ensure they can properly supply the required voltage for the loads.

## 5. What unit is apparent power measured in?

- A. Watts
- B. Volt-amps**
- C. Kilowatts
- D. Ohms

Apparent power is measured in volt-amperes, which is the correct unit of measurement for this electrical concept. Apparent power represents the product of the current flowing in a circuit and the voltage across it without taking the phase angle into consideration. This is particularly important in AC circuits, where the current and voltage can be out of phase due to reactive components like inductors and capacitors. While watts represents real power, which is the actual work done in a circuit, and kilowatts is a larger unit of measurement for real power, the key distinction lies in the understanding that apparent power encompasses both real power and reactive power. Ohms, on the other hand, are the units of resistance in electrical circuits and are not applicable to the measurement of power. Thus, volt-amps is the appropriate unit when discussing the total power in an electrical system, whether it is being used effectively or not.

## 6. In a large service installation, what type of transformers are contained within CT cans?

- A. Factor transformers
- B. Voltage transformers
- C. Current transformers**
- D. Phase transformers

In a large service installation, the type of transformers contained within CT cans are current transformers. Current transformers, or CTs, are specifically designed to measure the current flowing through a conductor. They do so by producing a secondary current proportional to the primary current, allowing for safe measurement without needing to directly connect measurement equipment to high voltage lines. Current transformers are crucial for monitoring and protection in electrical systems, as they enable the accurate transformation of high current levels to lower levels suitable for measuring instruments and relays, thus facilitating effective system management and safety. The presence of CTs within a dedicated can enclosure enhances their functionality and safety by offering protection from environmental factors and minimizing hazards associated with high current levels. This enclosure helps to ensure reliable operation while also making installation and maintenance easier. Other types of transformers, such as voltage transformers, are used to measure voltage levels, while factors and phase transformers serve different roles within electrical systems. Hence, the role and application of current transformers distinguish them within CT cans in large service installations.

**7. The peak-to-peak value of a sine wave is how many times the maximum positive peak value?**

- A. Once**
- B. Twice**
- C. Three times**
- D. Four times**

The correct answer is that the peak-to-peak value of a sine wave is twice the maximum positive peak value. To understand this, it's important to define what peak-to-peak value means in the context of a sine wave. A sine wave oscillates between its highest point, known as the maximum positive peak, and its lowest point, known as the maximum negative peak. The peak-to-peak value measures the total height of the wave from the maximum positive peak to the maximum negative peak. Since the maximum positive peak represents the highest value, and the maximum negative peak is equal in magnitude but opposite in sign, the distance from the highest to the lowest point (i.e., the peak-to-peak measurement) is simply the sum of the maximum positive and the absolute value of the maximum negative peak. Therefore, the peak-to-peak value is calculated as:

**Peak-to-Peak Value = Maximum Positive Peak + Absolute Maximum Negative Peak**

$= V_{max} + V_{max} = 2 * V_{max}$

This illustrates that the peak-to-peak value is indeed twice the maximum positive peak value, confirming the correctness of this answer. Understanding this relationship is crucial for analyzing waveforms in electrical engineering and related fields.

**8. What is the maximum phase angle between current and voltage in purely inductive or purely capacitive circuits?**

- A. 45°**
- B. 60°**
- C. 90°**
- D. 120°**

In purely inductive or purely capacitive circuits, the maximum phase angle between current and voltage is 90 degrees. This is a fundamental concept in AC (alternating current) circuit analysis. In a purely inductive circuit, the current lags the voltage by 90 degrees. This means that when the voltage waveform reaches its peak, the current is at zero, indicating that the two waveforms are out of phase. Conversely, in a purely capacitive circuit, the current leads the voltage by 90 degrees. Despite the difference in lead and lag, the magnitude of the phase angle between the two remains 90 degrees in both scenarios. This 90-degree phase relationship represents a completely reactive circuit where energy is alternately stored and released by the inductor or capacitor, without any real power being consumed. Thus, the correct answer reflects this key characteristic of phase relationships in purely inductive and capacitive circuits.

**9. Smaller transformers, typically 50 KVA and smaller, operating at or below 600 volts, are normally wound for what type of polarity?**

- A. Additive polarity**
- B. Subtractive polarity**
- C. Neutral polarity**
- D. Variable polarity**

Smaller transformers, particularly those rated at 50 KVA and below, and operating at or below 600 volts, are typically wound for additive polarity. Additive polarity means that when the primary and secondary windings are energized, the voltage in the secondary winding adds to the voltage in the primary winding. This is essential for proper operation and ensures that the transformers function correctly when used in parallel or when combining voltages. Proper additive polarity aligns with standard electrical practices, helping to prevent phase issues and voltage discrepancies during operation. In a practical application, using transformers with additive polarity simplifies the design and increases the reliability of electrical systems, especially in smaller scale applications where efficiency and accuracy are crucial. Understanding the importance of polarity in transformers is fundamental for successful electrical installations and maintenance.

**10. In a 60 Hz circuit with a 1.3 mH inductor, what is the inductive reactance in ohms after conversion?**

- A. 0.49**
- B. 0.25**
- C. 1.02**
- D. 3.14**

To determine the inductive reactance of a circuit, you use the formula:  $X_L = 2\pi f L$  where: -  $(X_L)$  is the inductive reactance in ohms, -  $(f)$  is the frequency in hertz (Hz), -  $(L)$  is the inductance in henries (H). In this case, we are working with a frequency of 60 Hz and an inductance of 1.3 mH (which is equal to 0.0013 H). Plugging in the values: 1. First, convert the inductance from millihenries to henries:  $L = 1.3 \text{ mH} = 1.3 \times 10^{-3} \text{ H}$  2. Substitute the values into the formula:  $X_L = 2\pi (60)(1.3 \times 10^{-3})$  3. Calculate:  $X_L = 2\pi (60) (0.0013) \approx 3.14159 \times$

# Next Steps

**Congratulations on reaching the final section of this guide. You've taken a meaningful step toward passing your certification exam and advancing your career.**

**As you continue preparing, remember that consistent practice, review, and self-reflection are key to success. Make time to revisit difficult topics, simulate exam conditions, and track your progress along the way.**

**If you need help, have suggestions, or want to share feedback, we'd love to hear from you. Reach out to our team at [hello@examzify.com](mailto:hello@examzify.com).**

**Or visit your dedicated course page for more study tools and resources:**

**<https://iecyear2pt3.examzify.com>**

**We wish you the very best on your exam journey. You've got this!**

**SAMPLE**