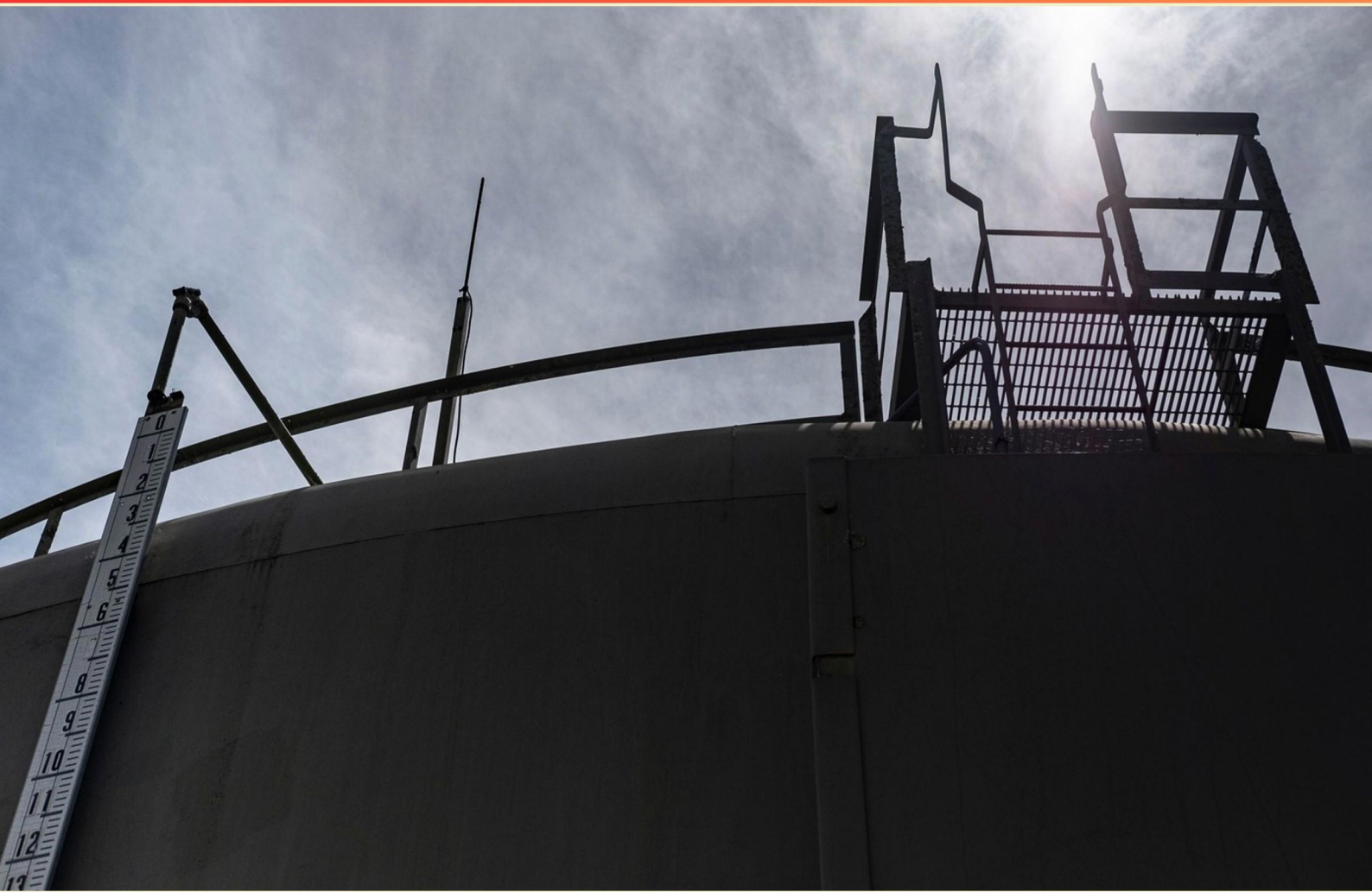


# OCC SACA SENSOR LOGIC SYSTEMS 1 (C-205) PRACTICE TEST (SAMPLE)

**STUDY GUIDE**



**SAMPLE STUDY GUIDE  
WITH LIMITED QUESTIONS**

**VISIT US ONLINE FOR  
THE FULL VERSION STUDY GUIDE**

<https://occsacac205.examzify.com>



**Copyright © 2026 by Examzify - A Kaluba Technologies Inc. product.**

**ALL RIGHTS RESERVED.**

No part of this book may be reproduced or transferred in any form or by any means, graphic, electronic, or mechanical, including photocopying, recording, web distribution, taping, or by any information storage retrieval system, without the written permission of the author.

Notice: Examzify makes every reasonable effort to obtain accurate, complete, and timely information about this product from reliable sources.

SAMPLE

# Table of Contents

|                             |    |
|-----------------------------|----|
| Copyright .....             | 1  |
| Table of Contents .....     | 2  |
| Introduction .....          | 3  |
| How to Use This Guide ..... | 4  |
| Questions .....             | 5  |
| Answers .....               | 8  |
| Explanations .....          | 10 |
| Next Steps .....            | 15 |

SAMPLE

# Introduction

Preparing for a certification exam can feel overwhelming, but with the right tools, it becomes an opportunity to build confidence, sharpen your skills, and move one step closer to your goals. At Examzify, we believe that effective exam preparation isn't just about memorization, it's about understanding the material, identifying knowledge gaps, and building the test-taking strategies that lead to success.

This guide was designed to help you do exactly that.

Whether you're preparing for a licensing exam, professional certification, or entry-level qualification, this book offers structured practice to reinforce key concepts. You'll find a wide range of multiple-choice questions, each followed by clear explanations to help you understand not just the right answer, but why it's correct.

The content in this guide is based on real-world exam objectives and aligned with the types of questions and topics commonly found on official tests. It's ideal for learners who want to:

- Practice answering questions under realistic conditions,
- Improve accuracy and speed,
- Review explanations to strengthen weak areas, and
- Approach the exam with greater confidence.

We recommend using this book not as a stand-alone study tool, but alongside other resources like flashcards, textbooks, or hands-on training. For best results, we recommend working through each question, reflecting on the explanation provided, and revisiting the topics that challenge you most.

Remember: successful test preparation isn't about getting every question right the first time, it's about learning from your mistakes and improving over time. Stay focused, trust the process, and know that every page you turn brings you closer to success.

Let's begin.

# How to Use This Guide

This guide is designed to help you study more effectively and approach your exam with confidence. Whether you're reviewing for the first time or doing a final refresh, here's how to get the most out of your Examzify study guide:

## 1. Start with a Diagnostic Review

Skim through the questions to get a sense of what you know and what you need to focus on. Your goal is to identify knowledge gaps early.

## 2. Study in Short, Focused Sessions

Break your study time into manageable blocks (e.g. 30 – 45 minutes). Review a handful of questions, reflect on the explanations.

## 3. Learn from the Explanations

After answering a question, always read the explanation, even if you got it right. It reinforces key points, corrects misunderstandings, and teaches subtle distinctions between similar answers.

## 4. Track Your Progress

Use bookmarks or notes (if reading digitally) to mark difficult questions. Revisit these regularly and track improvements over time.

## 5. Simulate the Real Exam

Once you're comfortable, try taking a full set of questions without pausing. Set a timer and simulate test-day conditions to build confidence and time management skills.

## 6. Repeat and Review

Don't just study once, repetition builds retention. Re-attempt questions after a few days and revisit explanations to reinforce learning. Pair this guide with other Examzify tools like flashcards, and digital practice tests to strengthen your preparation across formats.

There's no single right way to study, but consistent, thoughtful effort always wins. Use this guide flexibly, adapt the tips above to fit your pace and learning style. You've got this!

## Questions

SAMPLE

- 1. What is the recommended practice to verify controller expectations after swapping a sensor module?**
  - A. Never test the controller after swapping
  - B. Verify controller expectations by testing the input behavior under expected conditions and confirm the controller reads the change correctly
  - C. Assume compatibility without testing
  - D. Only update firmware
- 2. How inversion is created in sensor logic using normally closed contact?**
  - A. Place a normally closed contact in series with the coil; the coil energizes when the input is absent.
  - B. Place a normally closed contact in series with the coil; the coil energizes when the input is present.
  - C. Place a normally closed contact in parallel with the coil; coil energizes regardless.
  - D. Use a normally open contact to achieve inversion.
- 3. A capacitive proximity sensor uses the principle of what to sense objects?**
  - A. Inductance
  - B. Resistance
  - C. Capacitance
  - D. Reflectivity
- 4. Distinguish between analog sensor signals and digital (discrete) sensor signals and how logic handles them.**
  - A. Analog signals are binary; digital signals vary continuously.
  - B. Analog signals vary continuously and may require conditioning or ADCs; digital signals are on/off and map directly to logic inputs after conditioning.
  - C. Both analog and digital signals require no conditioning for PLC inputs.
  - D. Digital signals cannot be read by logic.
- 5. Why are relay contacts normally used to perform control logic?**
  - A. Relay contacts can turn some outputs on and others off at the same time
  - B. They are faster than microcontrollers
  - C. They require no maintenance
  - D. They produce less heat

- 6. Which statement best describes a common reference in PLC sensor wiring?**
- A. It is the data bus.
  - B. It is the shield only.
  - C. It is the reference path (ground) used by sensors and PLC.
  - D. It is the supply voltage only.
- 7. Which component is best to energize solenoids safely when there are multiple circuits?**
- A. Direct power
  - B. Pushbuttons
  - C. Fuses
  - D. Control relays
- 8. Before the mold on a plastic injection molding machine is pulled apart, a(n) \_\_\_\_\_ period must occur to allow the plastic to cool and harden.**
- A. Cooling
  - B. Dwell
  - C. Hold
  - D. Solidify
- 9. What component is used in a memory logic circuit?**
- A. Control relay
  - B. Input switch
  - C. Output indicator
  - D. Timer
- 10. Which element describes two or more normally closed switches in series?**
- A. NAND
  - B. NOT
  - C. NOR
  - D. AND

## **Answers**

SAMPLE

1. B
2. A
3. C
4. B
5. A
6. C
7. D
8. B
9. A
10. C

SAMPLE

## **Explanations**

SAMPLE

**1. What is the recommended practice to verify controller expectations after swapping a sensor module?**

- A. Never test the controller after swapping
- B. Verify controller expectations by testing the input behavior under expected conditions and confirm the controller reads the change correctly**
- C. Assume compatibility without testing
- D. Only update firmware

*When a sensor module is swapped, you need to revalidate what the controller expects by testing how the new sensor behaves under normal conditions and confirming that the controller reads the change correctly. This end-to-end check makes sure the controller sees the new sensor's signal within the expected range, uses the right scaling, and responds as intended. It also helps catch mismatches in wiring, sensor type, or timing that could cause incorrect control actions. Skipping testing or assuming compatibility can hide real issues, and updating firmware alone doesn't verify that the controller correctly interprets the new sensor input. The safest and most effective practice is to actively test the input behavior and verify the controller's readings and responses match what is expected with the new module.*

**2. How inversion is created in sensor logic using normally closed contact?**

- A. Place a normally closed contact in series with the coil; the coil energizes when the input is absent.**
- B. Place a normally closed contact in series with the coil; the coil energizes when the input is present.
- C. Place a normally closed contact in parallel with the coil; coil energizes regardless.
- D. Use a normally open contact to achieve inversion.

*Inversion in sensor logic means the output state is the opposite of the input condition. Using a normally closed contact in series with the coil does this: when the input is absent, the NC contact is closed and current can flow to energize the coil. When the input is present, the NC contact opens, cutting the current and de-energizing the coil. So the coil is ON when the input is OFF, and OFF when the input is ON, exactly the inverted behavior you want. Using a normally open contact in series would energize the coil only when the input is present (non-inverted). A normally closed contact in parallel could bypass the coil and yield unreliable results.*

**3. A capacitive proximity sensor uses the principle of what to sense objects?**

- A. Inductance
- B. Resistance
- C. Capacitance**
- D. Reflectivity

*Capacitive proximity sensors rely on changes in capacitance caused by the nearby object altering the electric field around the sensing electrode. The electrode and the object form a capacitor, and as the object approaches, the effective dielectric between the plates increases, raising the capacitance. The sensor's electronics detect this change (often by a shift in oscillation frequency or charging time) and signal when the object is close enough. This non-contact method is distinct from inductive sensing, which uses magnetic fields to detect metal objects, resistance-based sensing that needs a current path, or reflectivity-based sensing that relies on light.*

**4. Distinguish between analog sensor signals and digital (discrete) sensor signals and how logic handles them.**

- A. Analog signals are binary; digital signals vary continuously.
- B. Analog signals vary continuously and may require conditioning or ADCs; digital signals are on/off and map directly to logic inputs after conditioning.**
- C. Both analog and digital signals require no conditioning for PLC inputs.
- D. Digital signals cannot be read by logic.

*Analog signals come from sensors that vary smoothly over a range, so they can take an infinite number of values. To be read by logic, you usually condition them and convert the value to digital with an analog-to-digital converter (or use an analog input module that samples the signal). Digital (discrete) signals are two-state, on or off, and after conditioning to meet the logic voltage levels, they map directly to logic inputs and are read as distinct high or low states. This is why the best description says analog signals vary continuously and may require conditioning or ADCs, while digital signals are on/off and map to logic inputs after conditioning. The other statements mischaracterize analog as binary, claim digital can't be read by logic, or deny the need for conditioning in PLC inputs.*

**5. Why are relay contacts normally used to perform control logic?**

- A. Relay contacts can turn some outputs on and others off at the same time**
- B. They are faster than microcontrollers
- C. They require no maintenance
- D. They produce less heat

*Using a single relay coil to operate multiple contacts lets one control action change several circuits at once. The contacts can be wired so that some close (turn outputs on) while others open (turn outputs off) when the coil is energized, giving coordinated, multi-output control from one control signal. This ability to implement simple logic by arranging normally open and normally closed contacts in various paths makes relays ideal for control logic in many systems. They also provide isolation between the control and the load, but the key benefit is the capacity to drive multiple outputs simultaneously with one action.*

**6. Which statement best describes a common reference in PLC sensor wiring?**

- A. It is the data bus.
- B. It is the shield only.
- C. It is the reference path (ground) used by sensors and PLC.**
- D. It is the supply voltage only.

*In PLC sensor wiring, the common reference is the shared ground path that all sensors and the PLC inputs refer to. This ground provides the return current for sensor signals and a stable zero-volt reference so the PLC can interpret the input voltages correctly. Without a common ground, signals can float or drift, causing incorrect readings and noise or differences between devices. The data bus is about communication, not the signal reference. The shield protects against EMI, but it isn't the main signal reference path. The supply voltage powers devices, but it isn't the reference the inputs use to measure signals.*

**7. Which component is best to energize solenoids safely when there are multiple circuits?**

- A. Direct power
- B. Pushbuttons
- C. Fuses
- D. Control relays**

*Using a control relay lets you drive solenoids from a separate control circuit while keeping the power side isolated. The relay's coil can be powered by a small, safe control signal, while its contacts switch the heavier current needed by the solenoid. This isolation prevents cross-talk or backfeed between multiple circuits and reduces the risk that a fault on one circuit affects the others. It also lets you wire protection devices (like fuses) and suppression components on the load side without tying control and load together, and enables remote or interlocked operation. In short, a relay provides the safe, reliable way to energize solenoids across several circuits by separating control from load and handling the higher current with properly rated contacts.*

**8. Before the mold on a plastic injection molding machine is pulled apart, a(n) \_\_\_\_\_ period must occur to allow the plastic to cool and harden.**

- A. Cooling
- B. Dwell**
- C. Hold
- D. Solidify

*Dwell time is the pause in the molding cycle when the mold stays closed after the plastic is injected, allowing the material to cool and harden before the mold is opened. This brief waiting period lets the molten polymer solidify under pressure against the mold surfaces, so the part dimensions stabilize and you avoid distortion, sink marks, or ejection damage. If you open the mold too soon, the part may still be soft and deform, leading to poor quality. Cooling describes the overall heat loss process, not a specific pause. Hold refers to the packing pressure phase during or just after fill, not the cooling interval before ejection. Solidify describes the state of the part rather than the timed step in the cycle.*

**9. What component is used in a memory logic circuit?**

- A. Control relay**
- B. Input switch
- C. Output indicator
- D. Timer

*Memory in logic circuits relies on a device that can hold a state even after the triggering input is removed. A control relay fits this role because energizing its coil can change its contacts to latch the circuit, keeping the state until a reset occurs. This ability to "remember" a condition is what makes a relay a common memory element in simple sensor logic systems. An input switch only affects the circuit while pressed, so it doesn't store state. An output indicator merely shows the current state without memory. A timer introduces a delay but doesn't maintain a remembered state once the trigger ends.*

**10. Which element describes two or more normally closed switches in series?**

- A. NAND
- B. NOT
- C. NOR**
- D. AND

*Two normally closed switches in series behave like a NOR gate. Each NC switch is closed only when its controlling signal is off (false). When you put them in series, the current path exists only if both inputs are false, so the output is true only when neither input is true. If either input goes true, its NC contact opens and the circuit is broken, making the output false. That exactly matches the NOR behavior: true only when all inputs are false. So two or more normally closed switches in series describe NOR.*

SAMPLE

## Next Steps

Congratulations on reaching the final section of this guide. You've taken a meaningful step toward passing your certification exam and advancing your career.

As you continue preparing, remember that consistent practice, review, and self-reflection are key to success. Make time to revisit difficult topics, simulate exam conditions, and track your progress along the way.

If you need help, have suggestions, or want to share feedback, we'd love to hear from you. Reach out to our team at [hello@examzify.com](mailto:hello@examzify.com).

Or visit your dedicated course page for more study tools and resources:

<https://occsacac205.examzify.com>

We wish you the very best on your exam journey. You've got this!

SAMPLE